

Thunderbird Turn Signal

Submitted by: Piyusha Jahagirdar

In this lab, we designed a Finite State Machine(FSM) in System Verilog for controlling the taillights of Thunderbird.

Figure 1 shows the State Transition Diagram for the FSM

 


Figure 1

Table 1 is the for the FSM

Current State	F0	F1	F2	F3	F4	F5	F6	Next State
F0	0	1	0	0	0	0	0	F1
F1	0	0	1	0	0	0	0	F2
F2	0	0	0	1	0	0	0	F3
F3	1	0	0	0	0	0	0	F0
F0	0	0	0	0	1	0	0	F4
F4	0	0	0	0	0	1	0	F5
F5	0	0	0	0	0	0	1	F6
F6	1	0	0	0	0	0	0	F0

Table 1

Thunderbird_code.sv

--Code for thunderbird turn signal

```
module Thunder_bird(
```

```
input logic clk,  
input logic reset,  
input logic left, right,  
output logic l1,l2,l3,r1,r2,r3);  
enum int unsigned {s0,s1,s2,s3,s4,s5,s6} state,nextstate;  
always_comb  
  
begin  
case(state)  
    s0:  
        begin  
            l1=1'b0;  
            l2=1'b0;  
            l3=1'b0;  
            r1=1'b0;  
            r2=1'b0;  
            r3=1'b0;  
  
            if((left == 1'b0 && right == 1'b0) || (left == 1'b1 && right == 1'b1))  
                nextstate <=s0;  
            elsif(left == 1'b1 && right == 1'b0)  
                nextstate <=s1;  
            else  
                nextstate <=s4;  
            end  
  
    s1:  
        begin  
            l1=1'b1;
```

```
l2=1'b0;  
l3=1'b0;  
r1=1'b0;  
r2=1'b0;  
r3=1'b0;  
nextstate <= s2  
end
```

```
s2:  
  
begin  
l1=1'b1;  
l2=1'b1;  
l3=1'b0;  
r1=1'b0;  
r2=1'b0;  
r3=1'b0;  
nextstate <= s3  
end
```

```
s3:  
  
begin  
l1=1'b1;  
l2=1'b1;  
l3=1'b1;  
r1=1'b0;  
r2=1'b0;  
r3=1'b0;  
nextstate <= s0  
end
```

```
s4:
    begin
    l1=1'b0;
    l2=1'b0;
    l3=1'b0;
    r1=1'b1;
    r2=1'b0;
    r3=1'b0;
    nextstate <= s5
    end
```

```
s5:
    begin
    l1=1'b0;
    l2=1'b0;
    l3=1'b0;
    r1=1'b1;
    r2=1'b1;
    r3=1'b0;
    nextstate <= s6
    end
```

```
s6:
    begin
    l1=1'b0;
    l2=1'b0;
    l3=1'b0;
    r1=1'b1;
```

```
        r2=1'b1;
        r3=1'b1;
        nextstate <= s0
    end

    default:
        begin
            l1=1'b0;
            l2=1'b0;
            l3=1'b0;
            r1=1'b0;
            r2=1'b0;
            r3=1'b0;
            nextstate <= s0
        end

    endcase
end

always_ff@(posedge clk)
begin
    if(reset == 1'b1)
        state <= s0;
    else
        state <= nextstate
    end
endmodule
```

--Thunderbird_wrapper.sv

--rename signals to match LEDs and switches on DE2 board

```
Module wrapper(input logic[2:0] SW,  
               input logic [0:0] KEY,  
               output logic [2:0] LEDR,  
               output logic [7:5] LEDG);  
  
--use KEY0 for clk  
  
--switches for inputs  
  
--red and green LEDs for output  
  
Thunderbird Thunderbird(.clk(KEY[0], .reset(SW[0]),  
                          .left(SW[2]), .right(SW[1]),  
                          .la(LED[0], .lb(LED[1]), .lc(LED[2]),  
                          .ra(LED[5], .rb(LED[6]), .rc(LED[7]));  
  
Endmodule
```

Testing on the DE2 board

After compiling the code out next goal was to download the code on the DE2 board and test it on the FPGA chip. The pins on the FPGA will correspond to our input and output pins.

We toggled the switches SW[0], SW[1] and SW[2] to different input patterns. The output was displayed on the LED[0], LED[1], LED[2], LED[5], LED[6], LED[7].

Images of the output

